

Advanced Integrated Circuit Design Lab



TECHNISCHE
UNIVERSITÄT
DARMSTADT


Project Description BGR



Overview of the Design Task

Bandgap Reference based Voltage Reference (BGR)

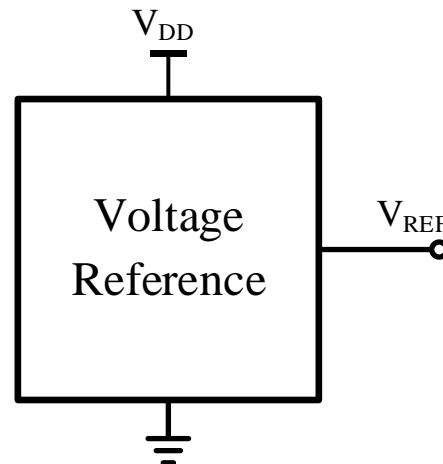Voltage references are used to produce constant voltages for other circuits in a system. In case of the audio amplifier IC which we are considering in this lab, the voltage reference is used to produce a common-mode reference voltage (V_{REF}) for the 8-Bit Successive-Approximation-Register-ADC (SAR-ADC) and the programmable gain amplifier (PGA).




BGR - Architecture

- The BGR circuit uses a Brokaw cell implementation to generate a reference voltage that is less sensitive to supply voltage, temperature and process variations.
- The circuit is based on the bandgap voltage of silicon to generate 1.205 V.
- This bandgap voltage can then be scaled to generate the reference voltage required for PGA and SAR_ADC.

The internal structure is depicted on the next slide.

Brokaw Cell Voltage Reference

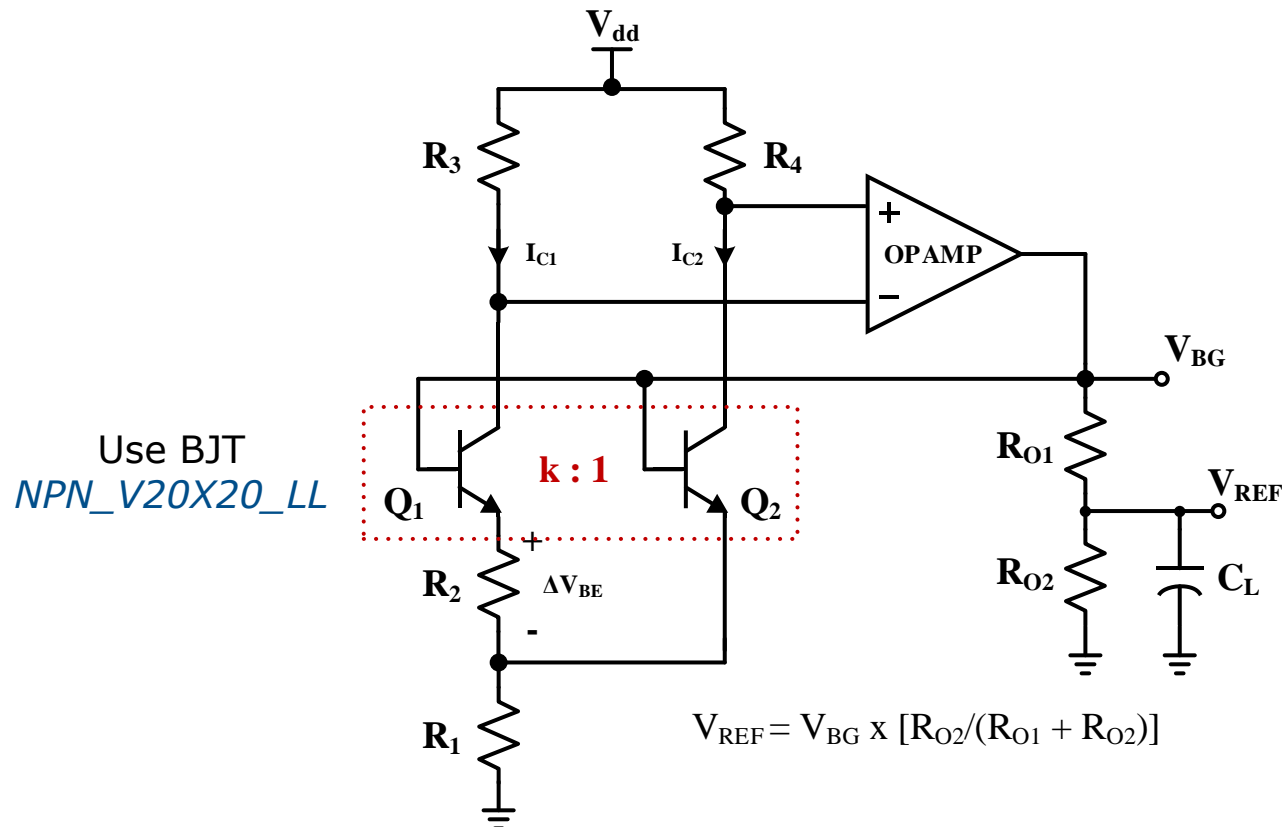- Use a Brokaw cell configuration to generate the bandgap reference voltage and from that in turn generate the 0.9 V reference voltage required for the PGA and SAR-ADC.




Brokaw Cell - Principle

- Temperature compensation
 - V_{BE} of a BJT decreases with temperature → Complementary to absolute temperature (CTAT).
 - $\Delta V_{BE} = V_{BE2} - V_{BE1}$ increases with temperature → Proportional to absolute temperature (PTAT).
 - The PTAT and CTAT characteristics are combined to compensate the temperature dependence of V_{REF} .
- Dimensioning
 - Emitter area's of Q_1 and Q_2 have a ratio of $k:1$.
 - The value of k was 8 for the originally proposed Brokaw cell [AD580 from Analog Devices].
 - The k needs to be adjusted for the technology being used → use simulations to find the k value for *umc65ll* technology with which you will be working in this lab.

Brokaw Cell – Generate V_{BG}

■ V_{BG}

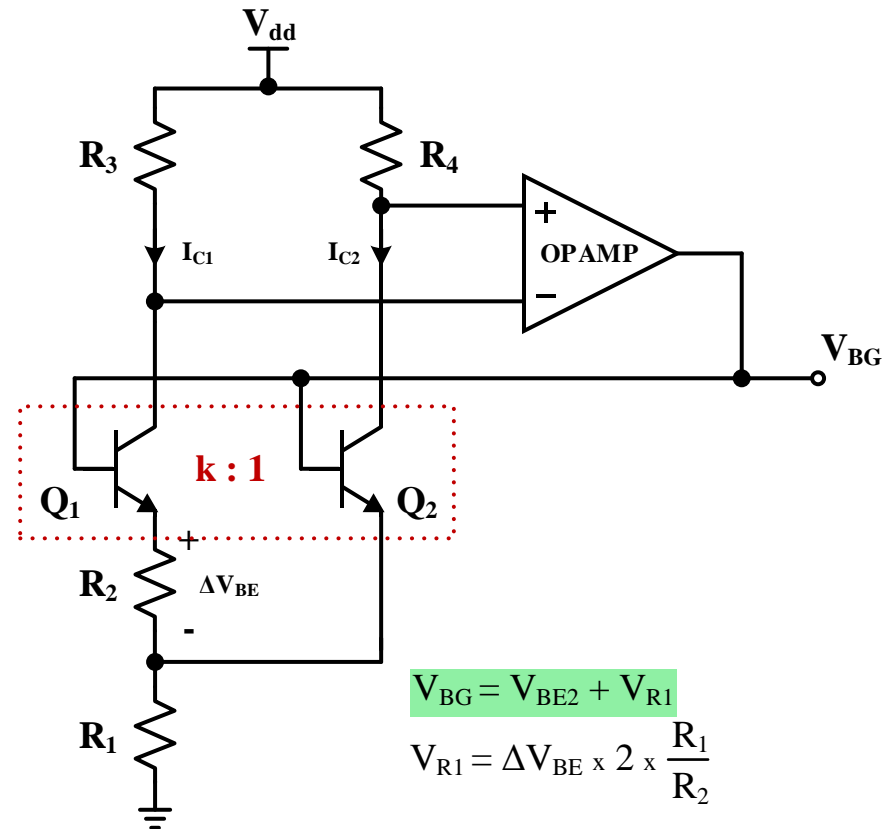
- $V_{BG} = 1.205 \text{ V}$.
 - Silicon bandgap voltage.
- Generated by compensating CTAT and PTAT behaviours.



Brokaw Cell – Startup

Startup-circuit

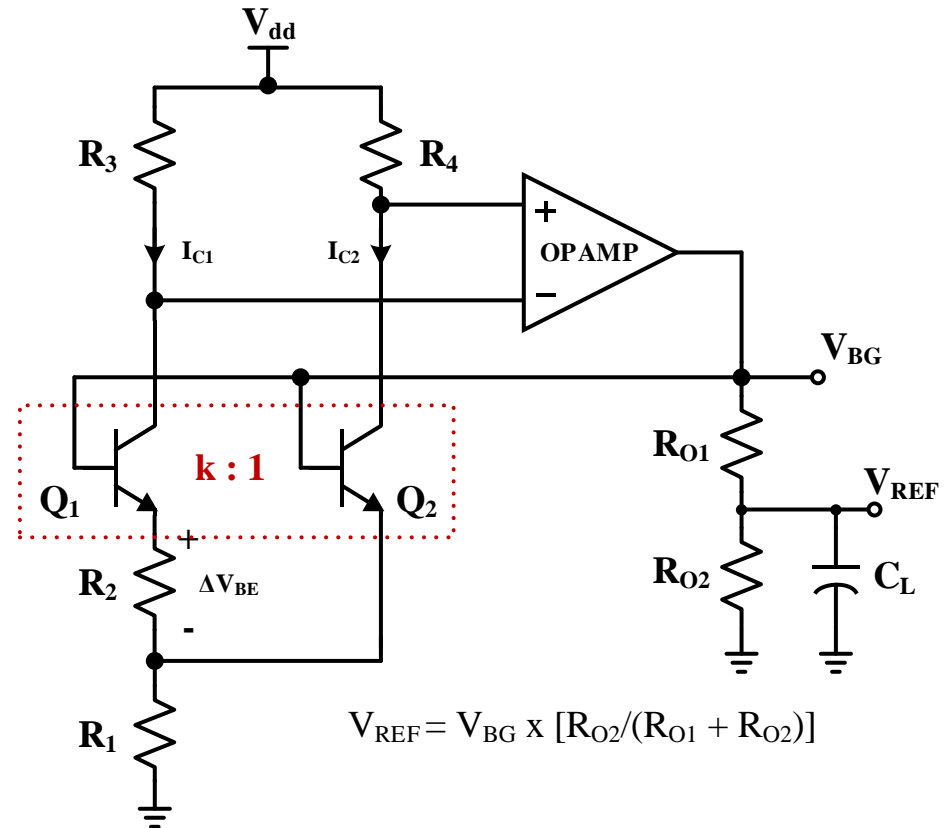- Intended operating point
 $V_{BG} \approx 1.205 \text{ V}$
- There can be another stable operating point:
 $V_{BG} \approx 0$ and $I_{C1} = I_{C2} \approx 0$
→ Add a circuit to avoid the undesired operating point



BGR - Specifications

- The below specifications have to be met for all corners (based on post-layout simulations):

Parameter	Unit	Specification
Reference Voltage (V_{REF})	V	0.9
Tolerance	%	< 3
Temperature Coefficient (TC) *	ppm/°C	< 100
DC Power Consumption	uW	< 1100
Power Supply Rejection Ratio (PSRR)	dB	> 40

* here defined as: $TC = \left| \frac{V_{max} - V_{min}}{T_{max} - T_{min}} \right|$ for the temperature range $T_{min} = 20^{\circ}C$ to $T_{max} = 40^{\circ}C$

- The Monte-Carlo simulations (no. of runs = 500) should satisfy the following (based on post-layout simulations):

Parameter	Unit	Specification
Standard Deviation for V_{REF}	%	< 1
Standard Deviation for TC	ppm/°C	< 50


BGR – Essential Information I

- Supply voltage
 - The single supply voltage is $V_{DD} = 1.8 \text{ V}$. Use *vdc* components from the *analogLib* library in simulations. In the hierarchical modules use components *vdd* and *gnd* to specify the global supply nets (see [Cadence_Virtuoso_Tutorial.pdf](#)).
- Corner analysis
 - The following corners need to be considered:

Corners		Range
Supply [V]		1.62, 1.98
Process Corners	mos	ff, fs, sf, ss
	res	ff, ss
	cap	ff, ss
	bjt	ff, ss
Temperature [°C]		0, 85

■ Simulations

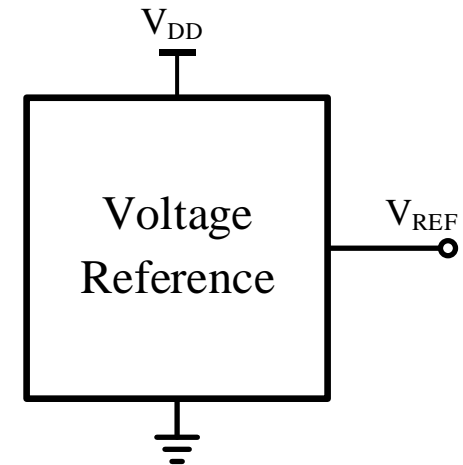- Use DC analysis for V_{REF} , TC, Tolerance and DC Power Consumption measurements.
- Use XF analysis for PSRR measurement.
- $V_{DD} = 1.8\text{ V}$.



■ Start-up Verification

- A start-up circuit should be implemented to ensure that the circuit behaves as expected after power on.
- Use transient analysis for start-up verification.
- Use a ramped supply with a rise time of 10 ms for the simulation.
 - Use *Vpulse* component from *analogLib* for this ramped supply.

Implementation Tips

Use *RNHR_LL* resistors. Avoid excessive resistance, keep it well below $< 1\text{M}\Omega$

Temperature coefficient can be optimized for operation at room temperature.

Your startup circuit should have a minimal influence during normal operation ($V_{BG} \approx 1.205\text{ V}$), but prevent the undesired operating point effectively.

Instructions for the testbench can be found in moodle.